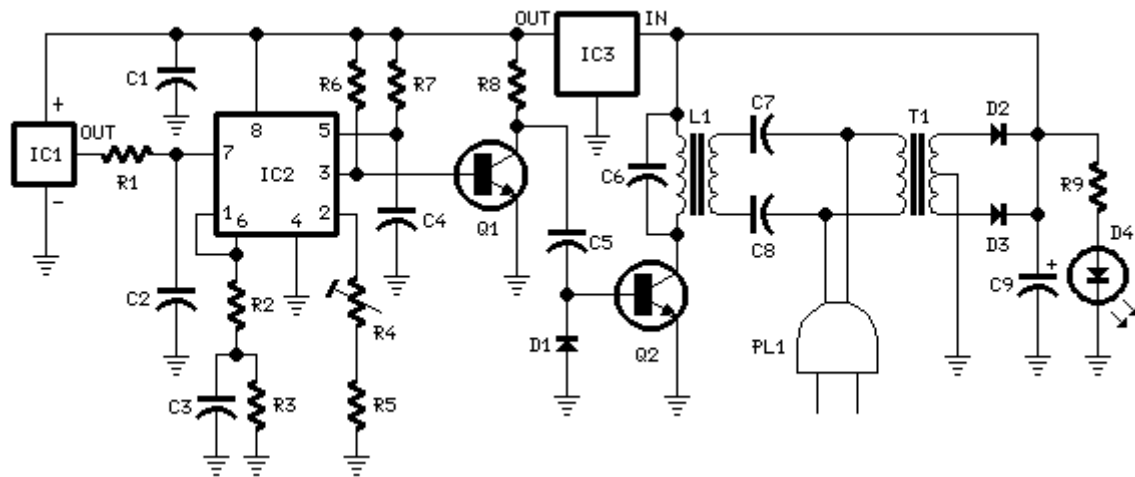


Digital Remote Thermometer

Remote sensor sends data via mains supply
Temperature range: 00.0 to 99.9 °C

Transmitter circuit diagram:



Transmitter parts:

R1,R3 _____ 100K 1/4W Resistors
R2 _____ 47R 1/4W Resistor
R4 _____ 5K 1/2W Trimmer Cermet
R5 _____ 12K 1/4W Resistor
R6 _____ 10K 1/4W Resistor
R7 _____ 6K8 1/4W Resistor
R8,R9 _____ 1K 1/4W Resistors

C1 _____ 220nF 63V Polyester Capacitor
C2 _____ 10nF 63V Polyester Capacitor
C3 _____ 1µF 63V Polyester Capacitor
C4,C6 _____ 1nF 63V Polyester Capacitors
C5 _____ 2n2 63V Polyester Capacitor
C7,C8 _____ 47nF 400V Polyester Capacitors
C9 _____ 1000µF 25V Electrolytic Capacitor

D1 _____ 1N4148 75V 150mA Diode
D2,D3 _____ 1N4002 100V 1A Diodes
D4 _____ 5mm. Red LED

IC1 _____ LM35 Linear temperature sensor IC
IC2 _____ LM331 Voltage-frequency converter IC

R3,R4,R6-R8__12K 1/4W Resistors
R5_____47K 1/4W Resistor
R9-R15_____470R 1/4W Resistors
R16_____680R 1/4W Resistor

C1,C2_____47nF 400V Polyester Capacitors
C3,C7_____1nF 63V Polyester Capacitors
C4_____10nF 63V Polyester Capacitor
C5,C6,C10___220nF 63V Polyester Capacitors
C8_____1000µF 25V Electrolytic Capacitor
C9_____100pF 63V Ceramic Capacitor

D1,D2,D5___1N4148 75V 150mA Diodes
D4,D4_____1N4002 100V 1A Diodes
D6-D8_____Common-cathode 7-segment LED mini-displays

IC1_____4093 Quad 2 input Schmitt NAND Gate IC
IC2_____4518 Dual BCD Up-Counter IC
IC3_____78L12 12V 100mA Voltage regulator IC
IC4_____4017 Decade Counter with 10 decoded outputs IC
IC5_____4553 Three-digit BCD Counter IC
IC6_____4511 BCD-to-7-Segment Latch/Decoder/Driver IC

Q1_____BC239C 25V 100mA NPN Transistor
Q2-Q4_____BC327 45V 800mA PNP Transistors

L1_____Primary (Connected to C1 & C2): 10 turns
 Secondary: 100 turns
 Wire diameter: 0.02mm. enameled
 Plastic former with ferrite core. Outer diameter: 4mm.

T1_____220V Primary, 12+12V Secondary 3VA Mains transformer

PL1_____Male Mains plug & cable

Device purpose:

This circuit is intended for precision centigrade temperature measurement, with a transmitter section converting to frequency the sensor's output voltage proportional to the measured temperature. The output frequency bursts are conveyed into the mains supply cables.

The receiver section counts the bursts coming from mains supply and shows the counting on three 7-segment LED displays. The least significant digit displays tenths of degree and then a 00.0 to 99.9 °C range is obtained.

Transmitter-receiver distance can reach hundred meters, provided both units are connected to the mains supply within the control of the same light-meter.

Transmitter circuit operation:

IC1 is a precision centigrade temperature sensor with a linear output of 10mV/°C driving IC2, a voltage-frequency converter. At its output pin (3), an input of 10mV is converted to 100Hz frequency pulses. Thus, for example, a temperature of 20°C is converted by IC1 to 200mV and then by IC2 to 20KHz. Q1

is the driver of the power output transistor Q2, coupled to the mains supply by L1 and C7,C8.

Receiver circuit operation:

The frequency pulses coming from mains supply and safely insulated by C1,C2 & L1 are amplified by Q1; diodes D1,D2 limiting peaks at its input. Pulses are filtered by C5, squared by IC1B, divided by 10 in IC2B and sent for the final count at the clock input of IC5.

IC4 is the time-base generator: it provides reset pulses for IC1B and IC5 and enables latches and gate-time of IC5 at 1Hz frequency. It is driven by a 5Hz square wave obtained from 50Hz mains frequency picked-up from T1 secondary, squared by IC1C and divided by 10 in IC2A.

IC5 drives the displays' cathodes via Q2,Q3 & Q4 at a multiplexing rate frequency fixed by C7. It drives also the 3 displays' paralleled anodes via the BCD-to-7 segment decoder IC6.

Summing up, input pulses from mains supply at, say, 2KHz frequency, are divided by 10 and displayed as 20.0°C.

Notes:

- | D6 is the Most Significant Digit and D8 is the Least Significant Digit.
- | R16 is connected to the Dot anode of D7 to permanently light the decimal point.
- | Set the ferrite cores of both inductors for maximum output (best measured with an oscilloscope, but not critical).
- | Set trimmer R4 in the transmitter to obtain a frequency of 5KHz at pin 3 of IC2 with an input of 0.5Vcc at pin 7 (a digital frequency meter is required).
- | More simple setup: place a thermometer close to IC1 sensor, then set R4 to obtain the same reading of the thermometer in the receiver's display.
- | Keep the sensor (IC1) well away from heating sources (e.g. Mains Transformer T1).
- | Linearity is very good.
- | **Warning!** The circuits are connected to 220Vac mains, then some parts in the circuit boards are subjected to **lethal potential!**. Avoid touching the circuits when plugged and enclose them in plastic boxes.