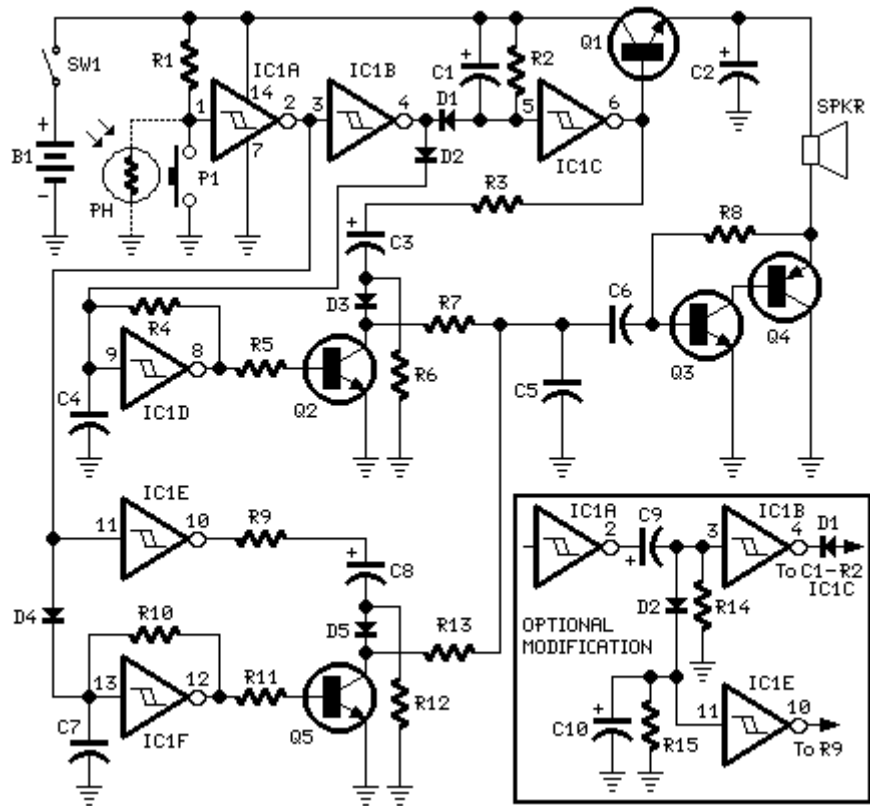


Bells ring Generator

Three circuit options
Can be synchronized to Christmas tree flashing lights

Circuit diagram:



Parts:

R1,R3,R7,R9,R13_10K	1/4W Resistors
R2_____1M5	1/4W Resistor
R4_____27K	1/4W Resistor
R5,R11_____47K	1/4W Resistors
R6,R12_____220K	1/4W Resistors
R8_____2M2	1/4W Resistor
R10_____33K	1/4W Resistor
C1_____2μ2	25V Electrolytic Capacitor
C2_____47μF	25V Electrolytic Capacitor
C3,C8_____10μF	25V Electrolytic Capacitors
C4,C7_____10nF	63V Polyester Capacitors

C5,C6_____100nF 63V Polyester Capacitors
D1-D5_____1N4148 75V 150mA Diodes
IC1_____MC14106 or 40106 Hex Schmitt Inverter IC
Q1_____BC337 45V 800mA NPN Transistor
Q2,Q3,Q5_____BC238 25V 100mA NPN Transistors
Q4 _____BC327 45V 800mA PNP Transistor
PH_____Photo resistor (any type) (see Notes)
P1_____SPST Pushbutton (see Notes)
SW1_____SPST Switch
SPKR_____8 Ohm Loudspeaker
B1_____3V Battery (two 1.5V AA or AAA cells in series etc.)

Parts added to optional modification:

R14_____220K 1/4W Resistor
R15_____1M 1/4W Resistor
C9_____4 μ 7 25V Electrolytic Capacitor
C10_____1 μ F 25V Electrolytic Capacitor

Device purpose:

This circuit generates a dual-tone bells ringing similar to most door-bell units. It can be used in many applications other than door-bell. In the Notes below several options will be given in order to suit different needs.

Circuit operation:

The circuit as shown in the diagram generates a "Ding-tone" when P1 is pressed and a "Dong-tone" when P1 is released. IC1D is the first-tone frequency generator and IC1F generates the second-tone. Q2, Q5 and related components act as shape and decay controls of the two tones, trying to imitate as close as possible the bells sound. Their outputs are mixed (R7 & R13), filtered (C5) and boosted by a simple class-A audio amplifier (Q3 & Q4) in order to drive the loudspeaker. The amplifier is switched-on by Q1 when P1 is pressed, then is switched-off some seconds after P1 is released: this time-delay is fixed by C1 & R2. In this manner the circuit draws a negligible current when in stand-by mode.

Notes:

- 1 To obtain a "Ding-Dong" operation when pushing on P1, no matter when it is released, you must

modify the circuit as shown in the frame placed at the low-right corner of the circuit diagram. D4 must be removed. C10 & R15 set the time-delay separating the first from the second tone.

- | To obtain a one-tone-only generator, wire the circuit as in the optional modification, making the following changes:

C9 = 100nF 63V Polyester Capacitor.

Omit R9 to R13 & R15; C7, C8 & C10; D2, D4, D5 & Q5.

Connect to negative supply pins 11 & 13 of IC1 and left open pins 10 & 12.

- | An amusing application of this circuit wired as in the original schematic, is to use a photo-resistor in place of P1, then placing the unit near the flashing lamps of your Christmas tree. A soft bell sound may be heard at switch-on and switch-off of the lamp chosen.
 - | To obtain higher output power you may substitute R8, Q3 & Q4 with an audio amplifier IC like the LM386 or LM380. In this case power supply must be raised to 6 - 12V but at the same time R4 & R10 should be changed to adjust bell-tone frequencies.
 - | Good tone frequencies are roughly 2000 and 1650Hz respectively.
 - | When in stand-by mode, current drawing of the circuit is 200 μ A @ 3V supply: therefore SW1 can be omitted.
-