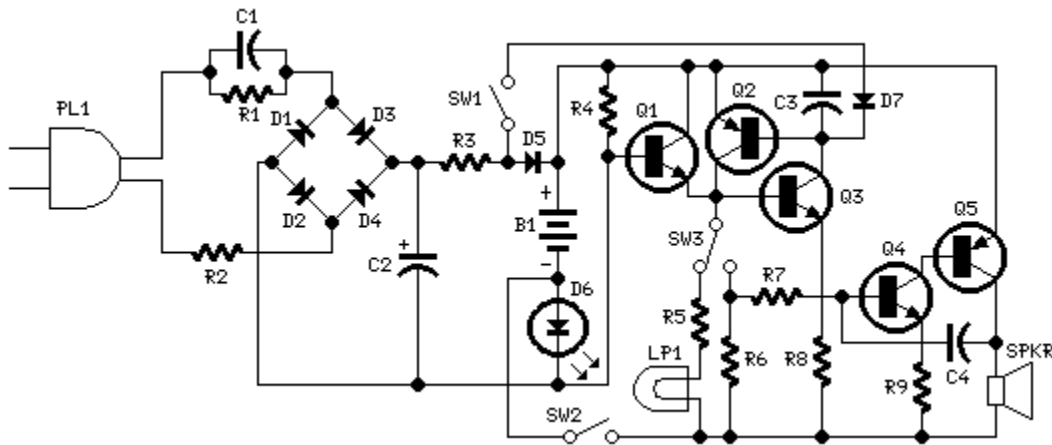


Emergency Light & Alarm

Powered by two AA NI-CD batteries
Four switchable options

Circuit diagram:



Parts:

R1	220K	1/4W Resistor
R2	470R	1/2W Resistor
R3	390R	1/4W Resistor
R4	1K5	1/4W Resistor
R5	1R	1/4W Resistor
R6	10K	1/4W Resistor
R7	330K	1/4W Resistor
R8	470R	1/4W Resistor
R9	100R	1/4W Resistor

C1	330nF	400V Polyester Capacitor
C2	10µF	63V Electrolytic Capacitor
C3	100nF	63V Polyester Capacitor
C4	10nF	63V Polyester Capacitor

D1-D5	1N4007	1000V 1A Diodes
D6	LED	Green (any shape)
D7	1N4148	75V 150mA Diode

Q1, Q3, Q4	BC547	45V 100mA NPN Transistors
Q2, Q5	BC327	45V 800mA PNP Transistors

SW1, SW2 _____ SPST Switches

SW3_____SPDT Switch

LP1_____2.2V or 2.5V 250-300mA Torch Lamp

SPKR_____8 Ohm Loudspeaker

B1_____2.5V Battery (two AA NI-CD rechargeable cells wired in series)

PL1_____Male Mains plug

Device purpose:

This circuit is permanently plugged into a mains socket and NI-CD batteries are trickle-charged. When a power outage occurs, the lamp automatically illuminates. Instead of illuminating a lamp, an alarm sounder can be chosen.

When power supply is restored, the lamp or the alarm is switched-off. A switch provides a "latch-up" function, in order to extend lamp or alarm operation even when power is restored.

Circuit operation:

Mains voltage is reduced to about 12V DC at C2's terminals, by means of the reactance of C1 and the diode bridge (D1-D4). Thus avoids the use of a mains transformer.

Trickle-charging current for the battery B1 is provided by the series resistor R3, D5 and the green LED D6 that also monitors the presence of mains supply and correct battery charging.

Q2 & Q3 form a self-latching pair that start operating when a power outage occurs. In this case, Q1 biasing becomes positive, so this transistor turns on the self latching pair.

If SW3 is set as shown in the circuit diagram, the lamp illuminates via SW2, which is normally closed; if set the other way, a square wave audio frequency generator formed by Q4, Q5 and related components is activated, driving the loudspeaker.

If SW1 is left open, when mains supply is restored the lamp or the alarm continue to operate. They can be disabled by opening the main on-off switch SW2.

If SW1 is closed, restoration of the mains supply terminates lamp or alarm operation, by applying a positive bias to the Base of Q2.

Notes:

- | Close SW2 **after** the circuit is plugged.
- | **Warning!** The circuit is connected to 220Vac mains, then some parts in the circuit board are subjected to **lethal potential!**. Avoid touching the circuit when plugged and enclose it in a plastic box.

This circuit was awarded with publication in ELECTRONICS WORLD "Circuit Ideas", September 2001 issue, page 708.
